

# Generalized Resistive Power Divider Design

By Greg Adams

This article presents a design method to achieve unequal power division at the output ports of a two-way resistive power divider

The resistive two-way power splitter, which divides an RF input signal equally between its two output ports, is well documented. This basic divider uses

the topology of Figure 1, with all three resistors having a value of  $Z_0/3$  [1].

The unequal divider of Figure 2 splits the input power unequally between its two output ports. Design equations have been published for this splitter, where ports 1, 2 and 3 are all matched to the same impedance  $Z_0$  [2].

A power splitter with the same topology as Figure 2 can be designed so that port 3 is matched to some impedance other than  $Z_0$ . There are two reasons to design the resistor network for a different impedance at port 3. First, it may be convenient in applications where, for instance, both 50 ohm and 75 ohm outputs are desired. Second, when the resistor network is designed for a port 3 impedance higher than  $Z_0$ , there will be less attenuation at port 3, resulting in unequal power at the output ports as well as different impedances.

For instance, if the splitter is designed for 3 dB loss at port 2, with all ports matched to 50 ohms, the attenuation at port 3 will be 15 dB. If we raise the port 3 impedance to 85 ohms, the attenuation at port 3 will only be 8.5 dB. If extreme bandwidth isn't needed, a reactive network can be used to transform the port 3 impedance back to 50 ohms if desired.

Using the circuit topology of Figure 2, resistor values may be chosen so that port 3 is matched to any impedance up to some maximum value. When the maximum allowable output impedance is chosen, the value of resis-

 


Figure 1 - Resistive power splitter.

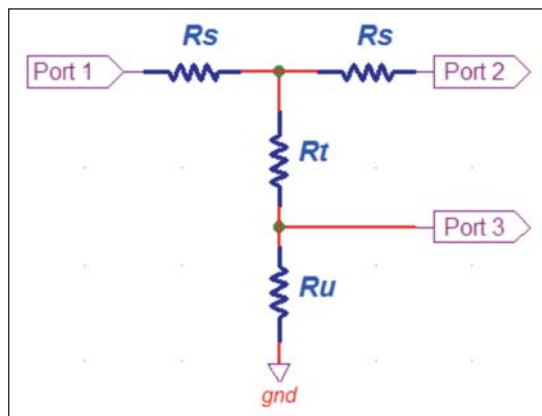


Figure 2 - Unequal resistive power splitter.

tor  $R_u$  becomes infinite, so that the network degenerates to the topology of Figure 1.

Design equations will be presented for an unequal power splitter where the port 3 impedance  $Z_1$  takes on any chosen value between zero and the maximum allowable value  $Z_{max}$ .

## Design Procedure

### Step 1:

Choose a value of attenuation, no greater than 6 dB, for output 1, and design the Tee

attenuator of Figure 3 for that attenuation value, where

$Z_0$  is the characteristic impedance.  
 $dB_{21}$  is the attenuation.  
 $\alpha$  is the voltage gain. ( $0.5 < \alpha < 1$ )

Given the value of  $S_{21}$ (dB), and normalizing  $Z_0$  to unity, we can solve for the resistor values  $R_s$  and  $R_p$ .

$$Z_0 = 1$$

$$\alpha = A \cdot \text{Log} \left( \frac{S_{21}(\text{dB})}{20} \right) \quad (1)$$

$$A = \left( \frac{1 - \alpha}{1 + \alpha} \right) \quad (2)$$

$$E = \left( \frac{1 - A^2}{2 \cdot A} \right) \quad (3)$$

$$R_s = A \cdot Z_0 \quad (4)$$

$$R_p = E \cdot Z_0 \quad (5)$$

**Step 2:**

At this point, we need to choose  $Z_0$ , the impedance at output port 2. Any value may be chosen up to a maximum,  $Z_{\max}$ . We'll compute  $Z_{\max}$  later.

**Step 3:**

Now, for  $R_p$ , we'll substitute the resistance of  $R_t$ , plus the parallel combination of  $R_u$  with the Port 3 load impedance  $Z_1$ . We require that the resistance of this network, from the top of  $R_t$  to ground, be equal to  $R_p$ . We also require that when ports 1 and 2 are terminated in  $Z_0$ , the resistance seen looking into port 3 be equal to  $Z_1$ . These two conditions are represented by two equations, which can now be solved for the two variables  $R_t$  and  $R_u$ . The following procedure will give the values of  $R_t$  and  $R_u$ .

$$A = R_s / Z_0 \quad (6)$$

$$D = Z_1 / Z_0 \quad (7)$$

$$E = R_p / Z_0 \quad (8)$$

$$F = E - (A + 1) / 2 \quad (9)$$

$$G = \frac{D \cdot A + D}{4} + \frac{E \cdot (D - A - 1)}{2} \quad (10)$$

$$T = \frac{-F + \sqrt{F^2 - 4 \cdot G}}{2} \quad (11)$$

 


Figure 3 · Tee attenuator circuit, designed according to equations 1-5.

$$U = \frac{1}{\frac{1}{E - T} - \frac{1}{D}} \quad (12)$$

$$R_s = Z_0 \cdot A \quad (13)$$

$$R_t = Z_0 \cdot T \quad (14)$$

$$R_u = Z_0 \cdot U \quad (15)$$

At this point, we have chosen values  $R_s$ ,  $R_t$  and  $R_u$ , which satisfy the conditions for a desired attenuation value from Port 1 to Port 2, and for all ports to be matched to the desired impedances  $Z_0$  and  $Z_1$ .

It remains to solve for  $Z_{\max}$ , the maximum allowable value of  $Z_1$ , and to find out what attenuation we are left with from Port 1 to Port 3.

**Step 4:**

It remains to find the maximum allowable value of  $Z_1$ . Recall that  $D = Z_1 / Z_0$ , so we'll be solving for the maximum value of  $D$ . From Equation 11, we see that the expression under the radical

$$F^2 - 4 \cdot G$$

must be greater than or equal to zero, if  $R_t$  and  $R_u$  are to have real values.

$Z_1$  will have its maximum allowable value ( $Z_{\max}$ ) and the attenuation from Port 1 to Port 3 will have its minimum possible value when

$$F^2 - 4 \cdot G = 0 \quad (16)$$

Since the variables  $F$  and  $G$  are functions of  $A$ ,  $D$  and  $E$  alone, we can solve Equation 16 for the value of  $D$ , knowing only  $A$  and  $E$ , which were determined in step 1.

This results in;

 


Figure 4 · Power splitter with an additional matching circuit on port 3. This can be used when a limited bandwidth is acceptable at port 3.

$$D_{\max} = Z_{\max} / Z_o = \frac{E^2 + E \cdot A + E + \frac{(A+1)^2}{4}}{A+1+2 \cdot E} \quad (17)$$

$S_{21}(\text{dB})$	$S_{31}(\text{dB})$ ( $Z_1 = Z_o$ )	$S_{31}(\text{dB})$ ( $Z_1 = Z_{\max}$ )	$Z_o$	$Z_{\max}$
1	-24.7758	-12.646487	50	229.887
2	-18.6824	-9.9209966	50	121.5529
3	-15.0135	-8.3775801	50	85.60054
4	-12.2482	-7.3958399	50	67.74285
5	-9.80391	-6.6125321	50	57.12214
6	-6.45451	-6.0339142	50	50.11901

Table 1 · Comparing  $S_{31}$  loss for  $Z_1 = Z_o$  vs.  $Z_1 = Z_{\max}$ .

**Step 5:**

Finally, we solve for  $dB_{S_{31}}$ , the attenuation from Port 1 to Port 3.

$$H = \frac{1}{\frac{1}{E} + \frac{1}{A+1}} \quad (18)$$

$$J = \frac{1}{\frac{1}{C} + \frac{1}{D}} \quad (19)$$

$$\beta = \frac{H}{(H+A) \cdot \frac{J}{J+T}} \quad (20)$$

$$S_{31} \text{ dB} = 10 \cdot \log\left(\frac{Z_1^2 \cdot Z_1}{Z_1}\right) \quad (21)$$

A couple of examples will illustrate the results that can be obtained:

*Example 1:* Unequal power splitter with 1 dB loss between ports 1 and 2, and all ports matched to 50 ohms:

- $Z_o = 50$  ohms
- $Z_1 = 50$  ohms
- $S_{21} = -1$  dB
- $S_{31} = -24.78$  dB
- $R_s = 2.87$  ohms
- $R_t = 406.8$  ohms
- $R_u = 56.52$  ohms

*Example 2:* Unequal splitter with 1 dB loss between ports 1 and 2,  $Z_o = 50$  ohms and  $Z_1 = 75$  ohms.

Notice that the loss at port 3 ( $-S_{31}$ ) is 2 dB lower than that of Example 1.

$Z_0 = 50$  ohms  
 $Z_1 = 75$  ohms  
 $S_{21} = -1$  dB  
 $S_{31} = -22.72$  dB  
 $R_s = 2.87$  ohms  
 $R_t = 392$  ohms  
 $R_u = 91.37$  ohms

*Example 3:* Unequal splitter with 1 dB loss between ports 1 and 2, and let  $Z_1$  have the maximum allowable value, to minimize the loss at port 3.

Notice that the loss at port 3 now has its lowest possible value at 12.56 dB.

$Z_0 = 50$  ohms  
 $Z_1 = 229.8$  ohms  
 $S_{21} = -1$  dB  
 $S_{31} = -12.64$  dB  
 $R_s = 2.87$  ohms  
 $R_t = 203$  ohms  
 $R_u = \text{Open Circuit}$

As illustrated in Figure 4, a simple L/C matching circuit can be added to the splitter of Example 3, to transform the 229.8 ohm impedance down to 50 ohms at port 3. This results in a splitter with equal impedance outputs, but with much less loss at port 3 than the splitter in example 1. The trade off is that this circuit only works over a limited bandwidth. To transform 229.8 ohms to 50 ohms, the inductor would have

a reactance of 95 ohms and the capacitor would have a reactance of 121 ohms at the operating frequency.

Table 1 compares the port 3 loss of the resistive network with all three ports matched to 50 ohms, versus a similar network with port 3 matched to the maximum allowable value of  $Z_1$ . It shows that when the  $S_{21}$  loss is small, the  $S_{31}$  loss can be reduced dramatically by increasing  $Z_1$ . When the  $S_{21}$  loss is close to 6 dB, little improvement in  $S_{31}$  can be achieved.

*Note:* A convenient “calculator” program can be found online at [www.flambda.com](http://www.flambda.com), to design power dividers according to the procedure above.

#### References:

1. D. Pozar, *Microwave Engineering*, John Wiley & Sons 1998, page 361.
2. D. Adams, “Designing Resistive Unequal Power Dividers,” *High Frequency Electronics*, March 2007.

#### Author Information

Greg Adams is an RF design engineer at a global security company. He has designed RF hardware for meteorological instruments, satcom, telemetry, radar and fiber communication systems over the past 30 years. He can be reached by e-mail at [gregory.f.adams@gmail.com](mailto:gregory.f.adams@gmail.com).

### High Frequency Electronics Online Archives



All past technical articles, informational columns and editorials are available for download in PDF format at this magazine’s web site. Articles are copyrighted, and may be used only for the personal use of the user. Any reprint, such as incorporation into a paper or presentation, may only be done with the permission of the publisher.

[www.highfrequencyelectronics.com](http://www.highfrequencyelectronics.com)